



Got Wireless? Modify a Simple 12VDC Wireless Remote Control for 5VDC Operation

Written By: Kevin Fodor



TOOLS:

- [Desoldering Braid \(1\)](#)
- [Desoldering Bulb \(1\)](#)
- [PanaVise \(1\)](#)
- [Soldering iron \(1\)](#)



PARTS:

- [Hookup wire, 22 AWG \(1\)](#)
- [Songle SRD-05VDC-SL-C 5VDC Relay \(1\)](#)
[optional, needed only if you intend to still use a relay as your output control](#)
- [RF Remote Control Transceiver and Receiver Pair \(1\)](#)
[Various Manufacturers and \(eBay\)](#)

SUMMARY

Adding a remote control switch to nearly any project is easy with these small keyfob-based RC relays. They are very inexpensive (<\$20) and offer such options as MOMENTARY and TOGGLE operation as well as multiple relay channels to control.

However, from what I found, these units require 12VDC to operate properly. This article explains how to convert one to use only 5VDC.

Additionally, a further mod converts this unit to provide a simple non-mechanical logic level, +5V/0v signal to use as an input to a micro-controller input or other circuit. This allows anyone to add a remote control switch capability to nearly any project, even if they don't need to control big loads through a relay.


In this short project I am going to explain the basics of these wireless control devices, explain which sections need to be hacked (changed) and finally how to test the modifications.

Step 1 — Overview



- Shown here is a typical unit you will find on [eBay](https://www.ebay.com) and other discount online outlets. It basically involves both a transmitter (keyfob) and receiver. The transmitter is typically a single-button keyfob but depending on the model purchased it may have more buttons and thus more channels.
- The receiver is made up of two parts; the RF front end and the decoder. Both are packaged together in the same enclosure.
- Both boards are compactly mounted in a small plastic box which makes it incredibly convenient to include and isolate within your own projects. Or you can remove the plastic enclosure altogether.

Step 2 — Initial Checkout

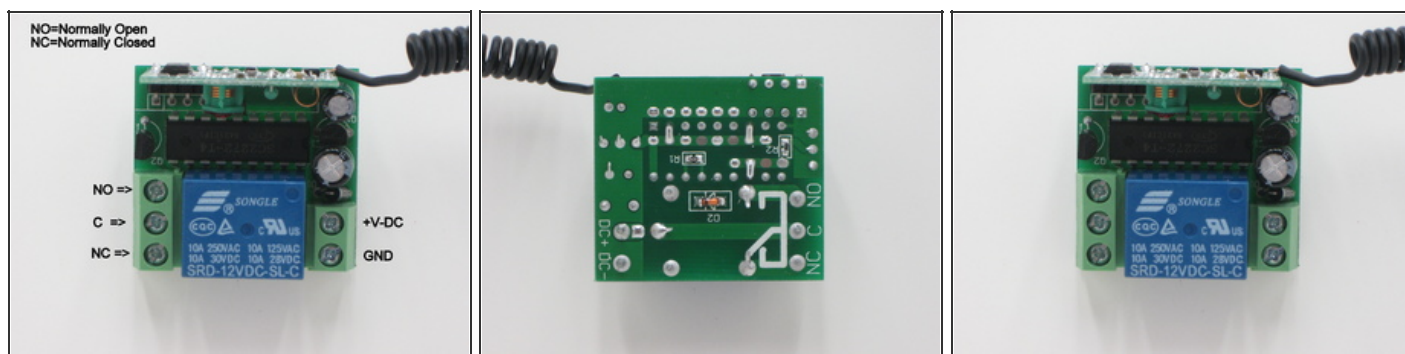

- Before making any modifications it is probably best to verify that the unit works as expected. The unit here is a 12VDC operated version which acts as a remote **MOMENTARY** switch. The relay used to control a load has Normally-Open (NO) and Normally-Closed (NC) contacts.
- Try connecting a simple load (a lamp) to the relay contacts and see that when the transmitter button is pressed the light turns on.




Step 3 — Identify the Parts



- Now we need to hack the module so that it can operate from 5VDC rather than 12VDC. But first let's identify the parts involved.
- Pull out the receiver PCB from the plastic case and place it into a vise.
- Locate the 12VDC relay and 78L05 voltage regulator; both of which we will be removing.
- On this board the voltage regulator is labeled as Q1 and will be in a 3-pin TO-92 package.
- The relay is the big blue 5-pin object in the center.



Step 4 — De-Solder the Relay

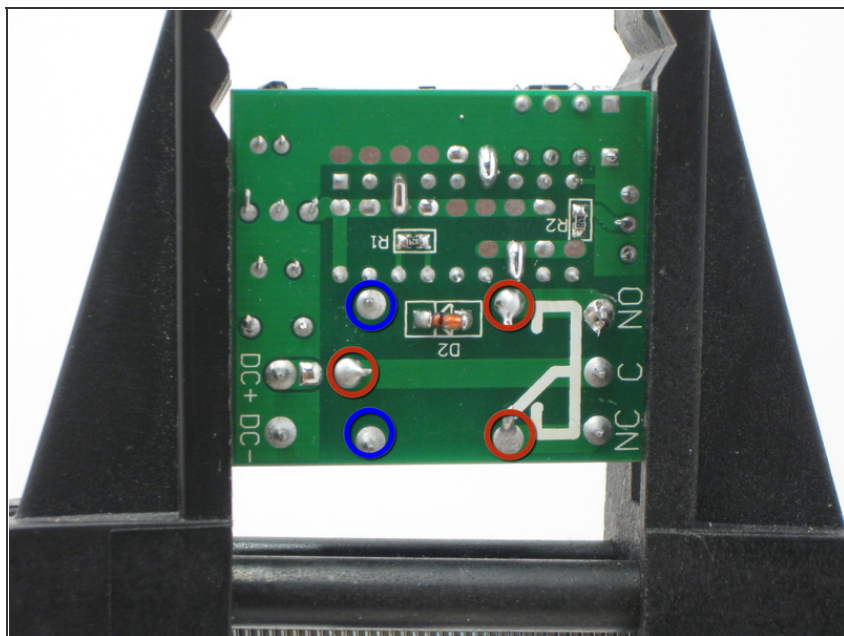

- Flip the PCB over and locate the 5 pins of the 12VDC relay.
- There are 5 pins on this relay that must be de-soldered. The blue markers indicate where the relay coil pins are. The red marks indicate the relay contact points.
- Heat each of the pins and use a solder bulb and wick to clean out all the solder holding the part in place.
- Gently pry the part off the PCB carefully.




Step 5 — Inspect Your Work

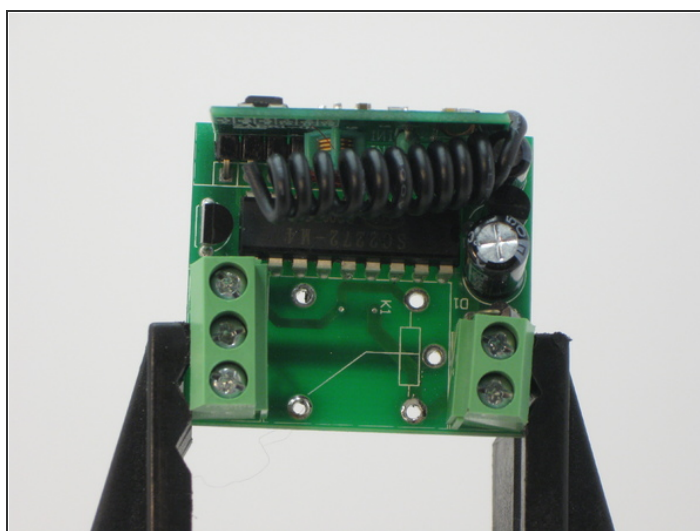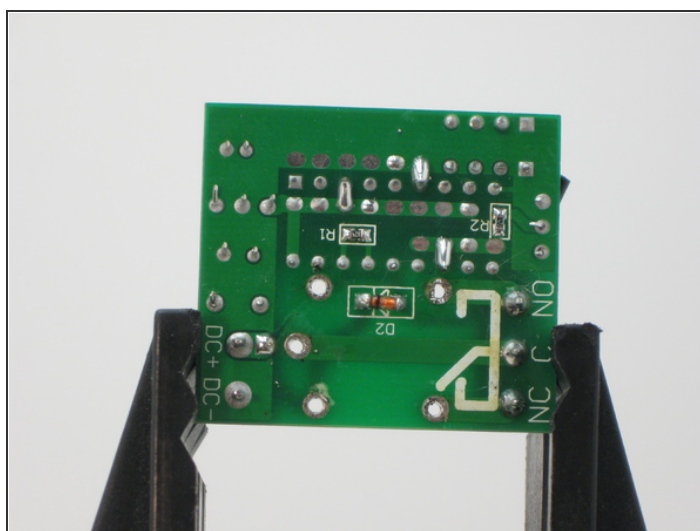

- Shown here is the PC board with the de-soldered relay removed. Make sure the holes are completely cleaned of solder.

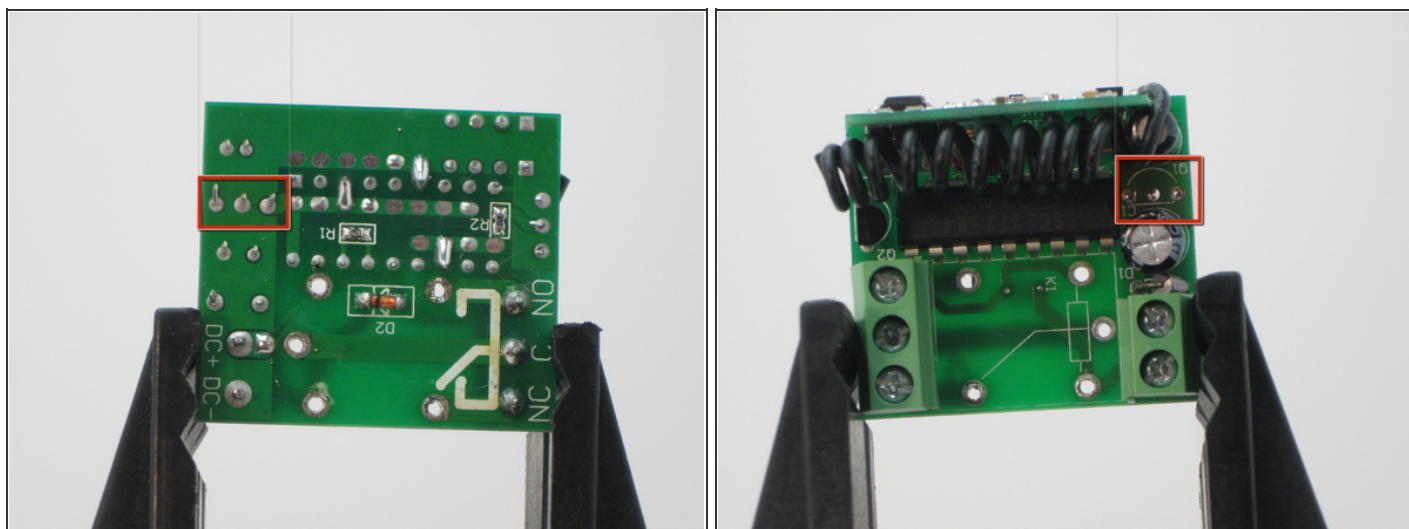
Step 6 — Remove the Voltage Regulator (Q1)



- Now locate the 78L05 voltage regulator. This part is labeled Q1 and shown in the photo with a red rectangle.
- Desolder using a desoldering bulb and wick. Remove solder from all 3 pins of the TO-92 package.
- Gently remove the regulator. If you have trouble you can cut the leads. Just be sure to keep the PCB traces intact and not apply too much heat.



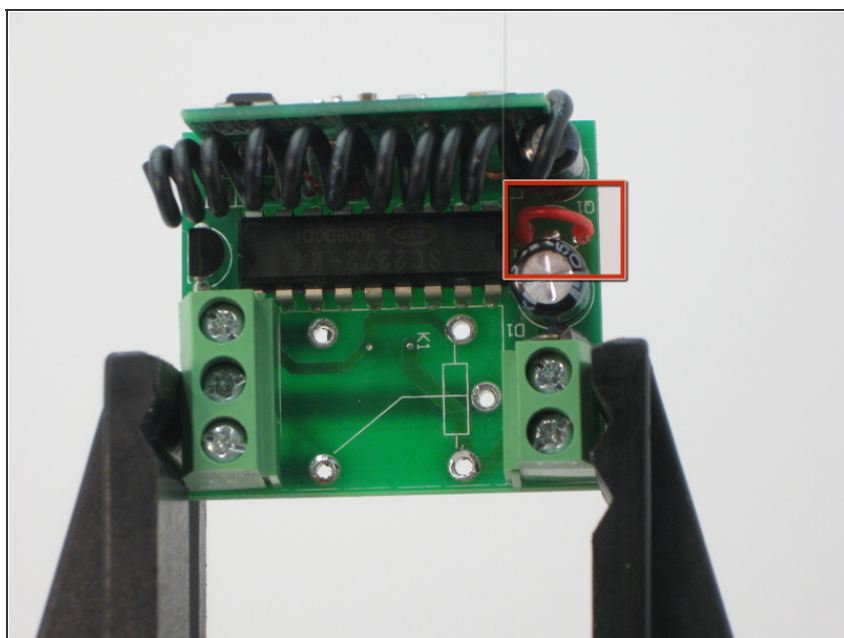
Step 7 — Short the Voltage Regulator Pins



- Insert a jumper wire between pin 1 and pin 3 of the 78L05. This will effectively take the input voltage and provide it directly to the output. The middle pin is already connected to ground.
- Be careful choosing a new 5VDC supply for this circuit as it now must be a regulated 5VDC supply. There is no longer any on-board voltage regulation.



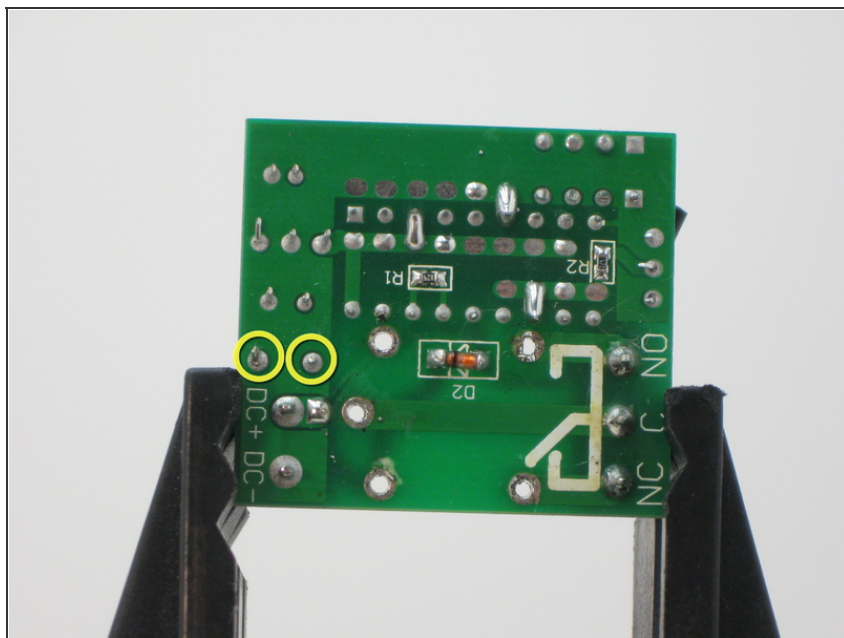Step 8 — Remove and Short Reverse Voltage Protection Diode.



- Desolder the 1N4007 diode located above the DC power input terminal block. If you don't do this you will lose about 1.0V from your power supply (so a 5V input results in only 4V to the circuit).
- Solder a wire between the two diode terminals in place where the diode was.
- Again, keep in mind that by doing this your module no longer has reverse input voltage protection...so be careful.



Step 9 — Project Variations


- Variation #1: If you have decided that this receiver needs to be able to continue to control a relay to drive the intended load, continue to step #10.
- Variation #2: If you have decided that this receiver needs to be able to drive a logic control signal instead, continue to step #12.

Step 10 — Project Variation #1: Replace Relay with 5VDC Operating Relay




- This variation will show you how to modify the module so that it operates a 5VDC relay in response to the transmitter button being pushed.
- Here we show a SONGLE SRD095VDC-SL-C 5VDC relay we are going to replace the previous 12V relay with. Notice that the footprint is identical.

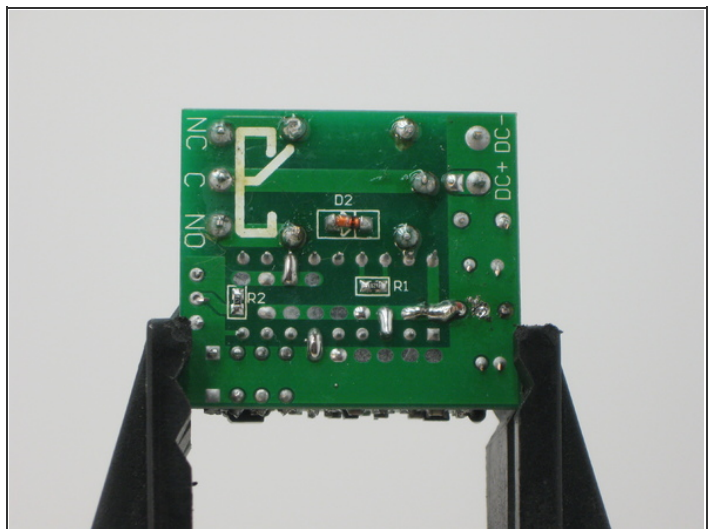Step 11 — Project Variation #1: Install the New Relay




- Place new 5VDC relay into the same position the 12VDC relay was in.
- Flip over the PCB and solder it into place.
- Now proceed to step #14 - Testing.

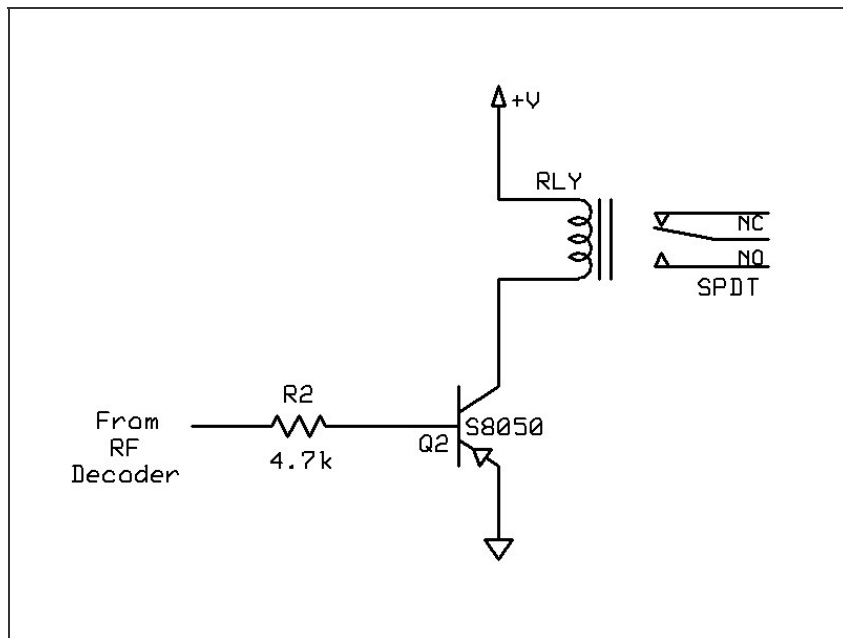Step 12 — Project Variation #2: Modify to Provide A Logic Signal Output

- This variation will show you how to modify the module so that it outputs a logic control signal in response to the transmitter button being pushed.
- The photo to the left shows a simplified version of the output driver for the relay from the RF decoder. Since we removed the relay I am going to show you how to modify this circuit to output a logic control signal instead.
- The PNP transistor (Q2) is used to drive the relay. Instead of driving a relay we are going to tap off of this output.

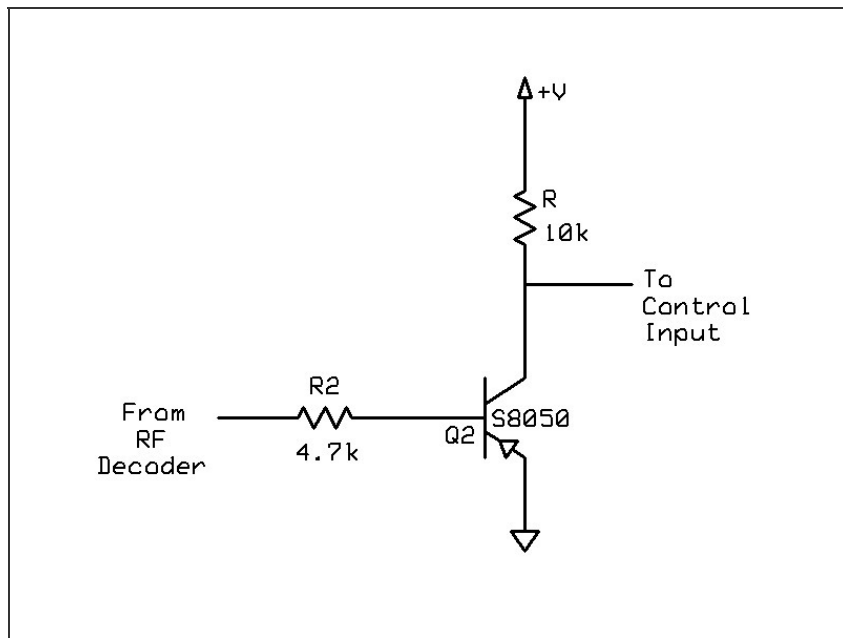
Step 13 — Project Variation #2: Circuit Modification



- The photo on the left shows that we need a pull-up resistor from Q2's collector pin to the supply voltage. This resistor (R) goes in place where the relay coil used to be.
- The collector pin from the S8050 PNP transistor now provides us with a logic control signal output.
- When the transmitter button is pressed Q2 turns on and the control signal is low (0V).
- When the transmitter is not pressed Q2 is off and the control signal is high (+5V).
- If the circuit you are trying to drive doesn't already have a pull-up resistor, you will need one (typically 10k) to pull the output high when the transistor is not on. But if your circuit already has a pull-up you do not need to install one.




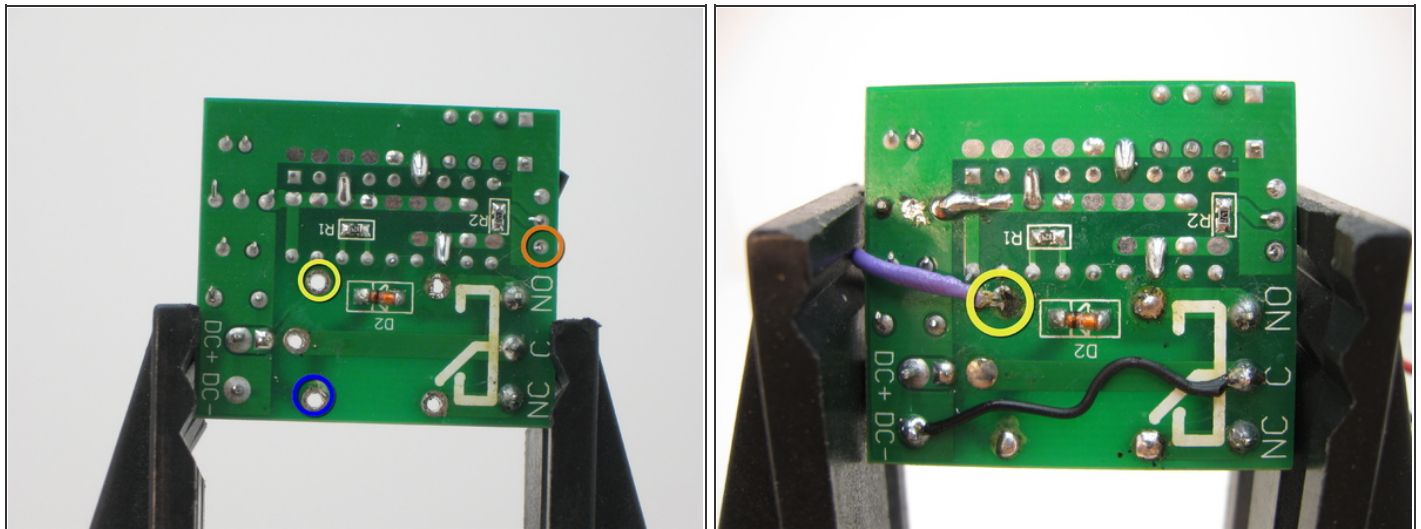
Step 14 — Project Variation #2: PCB Modification





- The photo to the left shows the connections on the PCB we are concerned about.
- The yellow marker shows the collector side of the relay coil. This is where we will tap off our logic control output signal.
- The blue marker is the relay coil's +V supply (which is now going to be +5V).
- The orange marker indicates where the Q2 collector pin is located. It is also electrically connected to the yellow marker as well.
- Remember, you do not need a pull-up resistor if your circuit already has one. In my case the circuit I intended to drive already had a pull-up resistor, so I did not install one here.

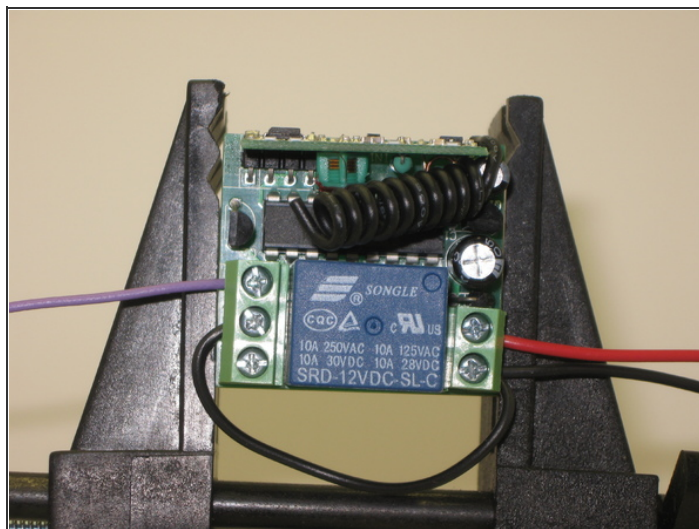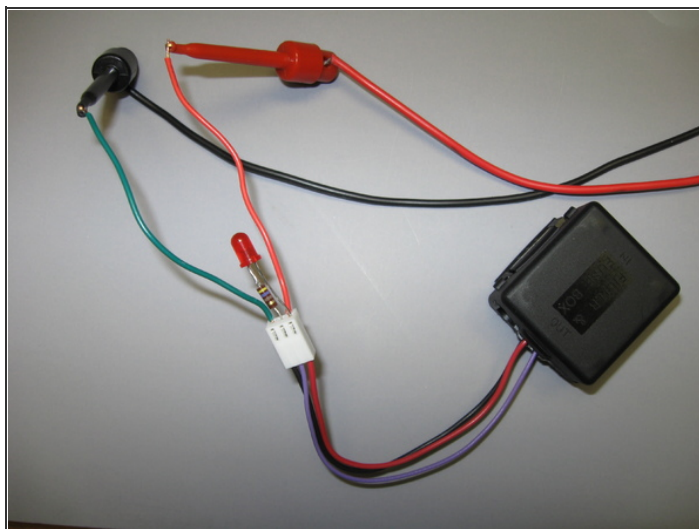


Step 15 — Test



- Test your modification, but be sure to only apply 5VDC for now on to the input terminals (there is no longer a voltage regulator in place, so be careful). The test here is shown with the relay modification, but the same idea is applicable with the logic signal modification as well. 
- Attach the output wires and any connectors you need to use. You can use either the normally open or normally closed output to test.
- In this photo you can see I am simply applying a 5VDC power source and I am checking that I can remotely operate the small LED using the transmitter.
- The second photo shows how I wired up my test circuit inside. In this example I tied the common connection from the relay to ground and the normally open connection to the LED's cathode. The anode of the LED was connected to the +5V supply via a current-limiting resistor (~1k).
- This allowed me to test operation by pressing the button and observe that the LED would turn on.
- By the way, I also added a small Molex connector which I will use to provide power to the module and receive the signal from the module. This connector is available at  [Mouser](#) and other electronics suppliers. [Click Here For Connector Parts](#).

Step 16 — Finished!

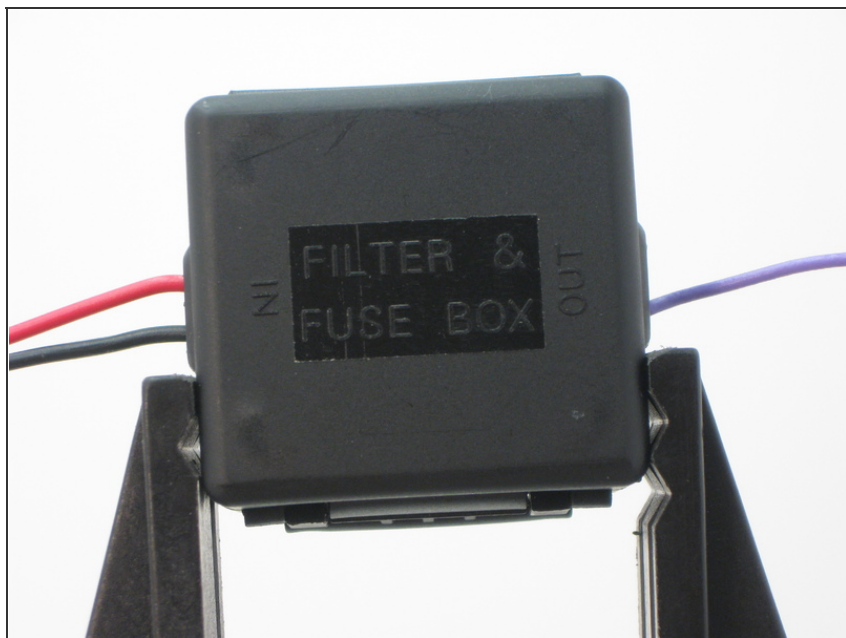

- That's it! You're done. Now all you need to do is mount it in the enclosure of your own project.
- With certainty this hack voids the warranty, which makes it even more fun to be able to modify something in such a way to use it as it was not originally intended.

After using these instructions you will be able to convert a 12VDC operated wireless switch to a 5VDC operated one with either a relay or logic level +5V/0V output.

This document was last generated on 2012-11-01 08:06:14 AM.